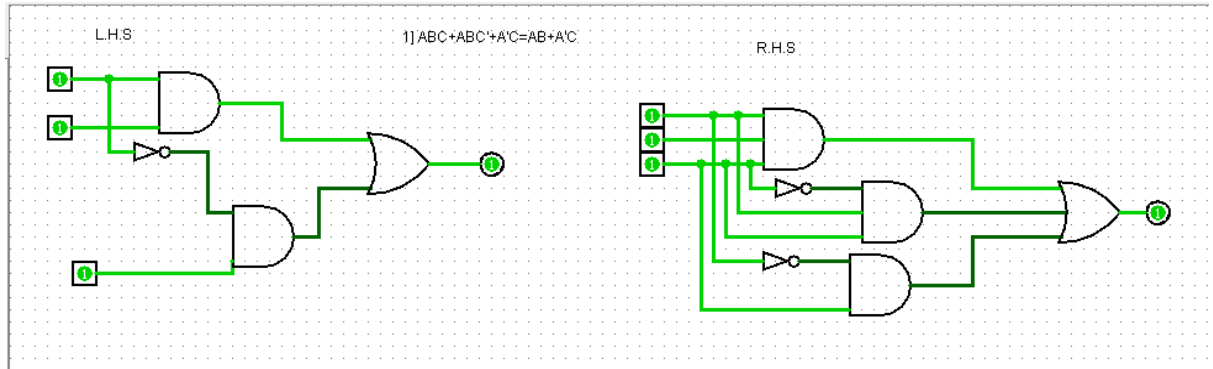


SHETH L.U.J AND M.V COLLAGE  
DSA (BOOLEAN ALGEBRA )  
PRATICAL NO 2


AIM:- BOOLEAN EXPRESSION SIMPLIFICATION;

Simplify given Boolean expressions and realize them using Logisim


1)  $ABC + ABC' + A'C = AB' + A'C$




2)  $AB' + CD + AB' + CD = AB' + C'D$

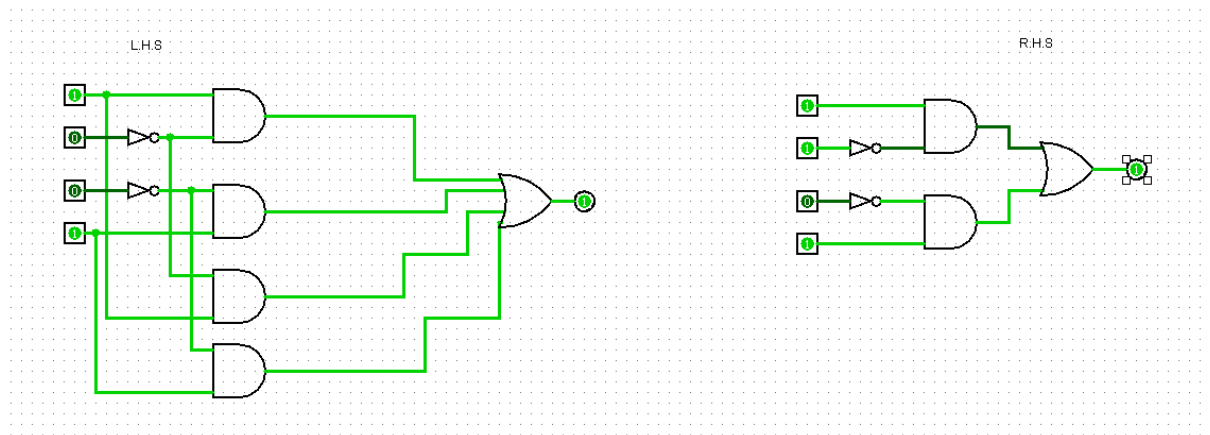

3)  $A + A'B = A + B$

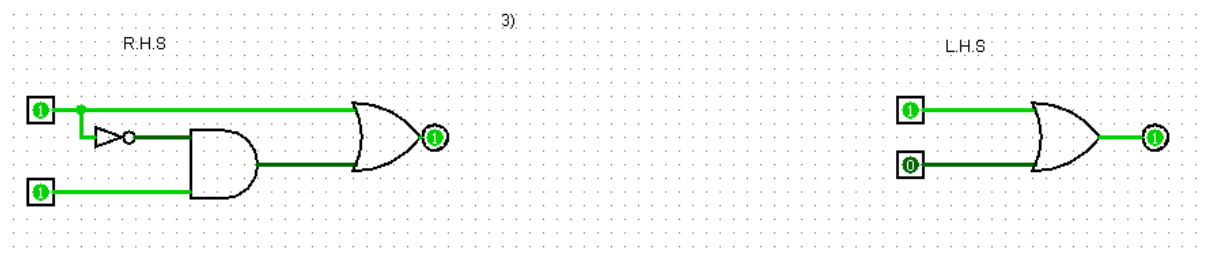


4)  $[(A + B')(B + C)]B = AB$

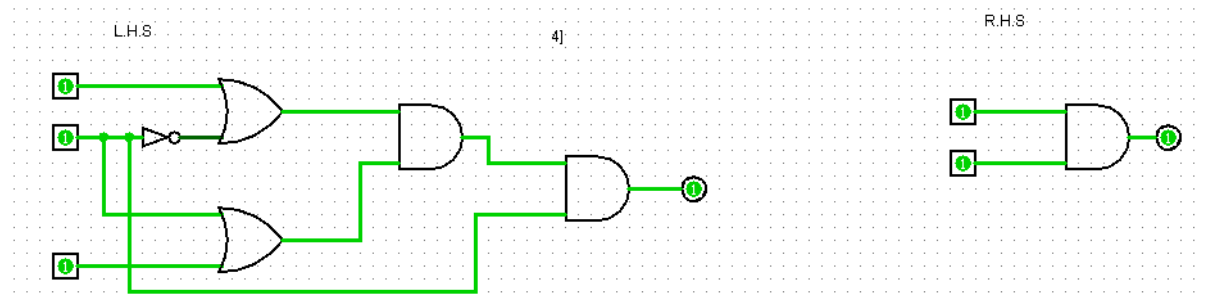


SHETH L.U.J AND M.V COLLAGE  
DSA (BOOLEAN ALGEBRA )  
PRATICAL NO 2

5]  $(A B C)' = A' + B' + C'$

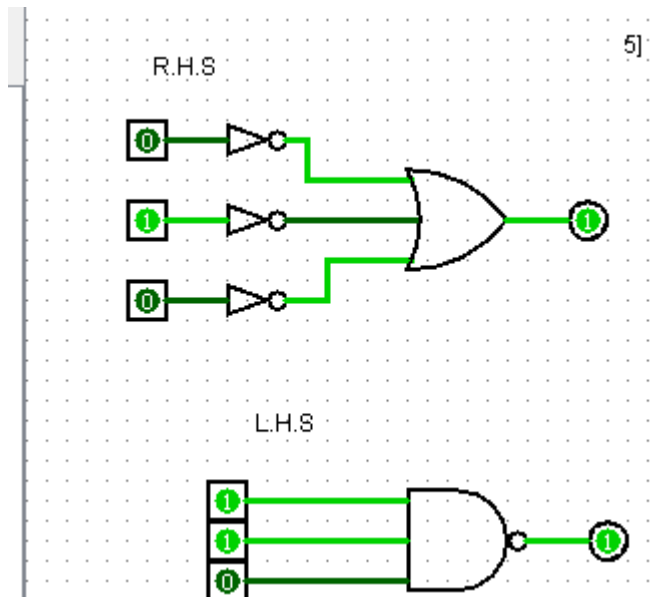

6]  $(A + B + C)' = A' B' C'$

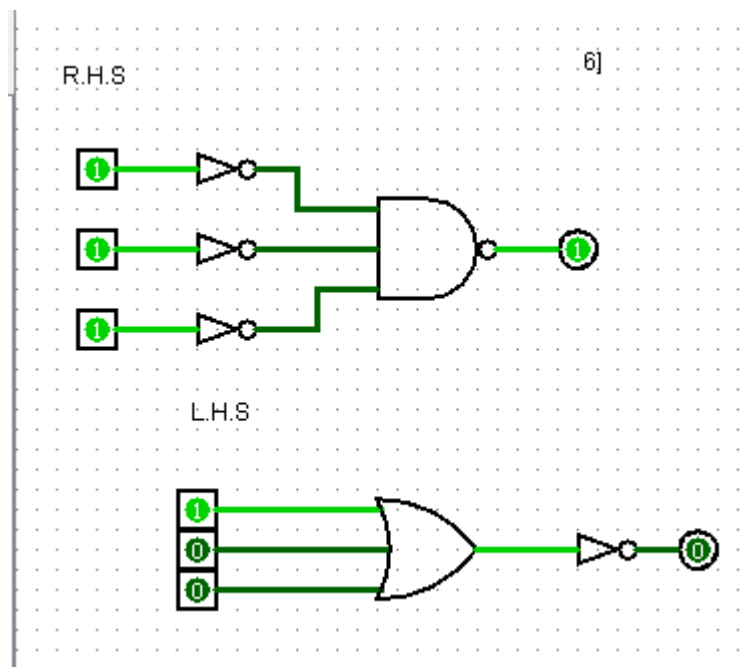

SHAIKH SAMMRIN

F113